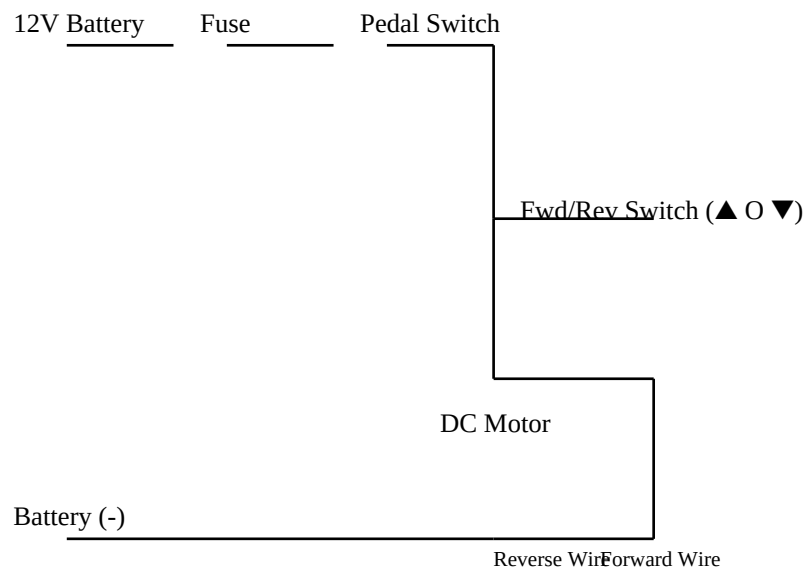


Kids Ride-On Car Forward/Reverse Switch and Pedal Wiring Diagram

This diagram explains how the forward/reverse selector switch (▲ O ▼) and pedal switch work together to control the 12V DC motor in a kids' ride-on car. The system allows movement in forward or reverse direction based on the toggle switch position, while the pedal acts as the power trigger.



Operation:

1. When the pedal is pressed, current flows from the battery through the fuse and pedal switch.
2. The direction (Forward or Reverse) depends on the toggle switch position:
 - ▲ = Forward direction
 - ▼ = Reverse direction
 - O = Neutral (no movement)
3. The motor runs in the chosen direction until the pedal is released.